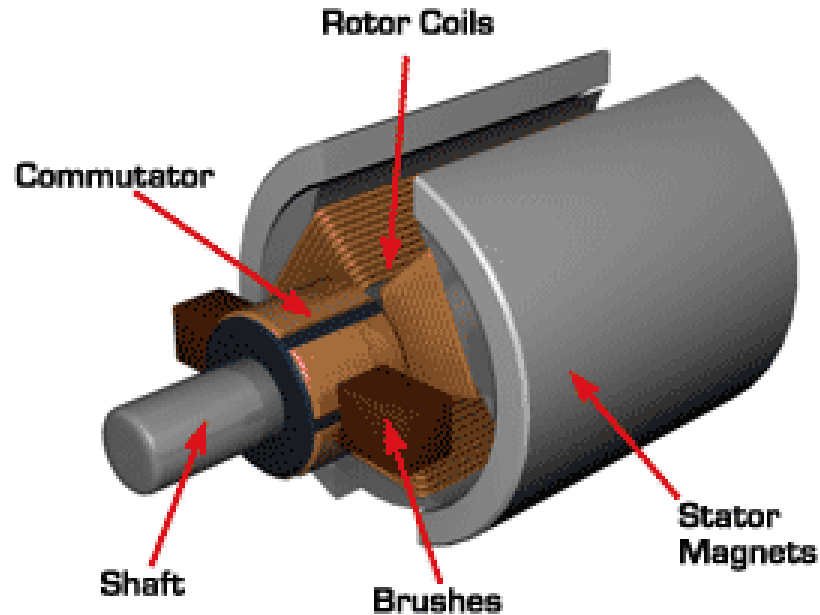


Electrical Engineering I

Machines Lab Assessment: DC Motor: Voltage Control and H-Bridge



Dr John Arvanitakis
ac7632@coventry.ac.uk


- Speed Control: Speed variation is accomplished by changing either the armature voltage or field voltage, or a combination of both.
- Constant Torque: Supplies constant torque over a wide speed application




- Simplest form of DC Motor
- Stator armature is substituted by permanent magnets
- Reduced size, applications in various fields (robotics etc.)

Applications of DC Motors

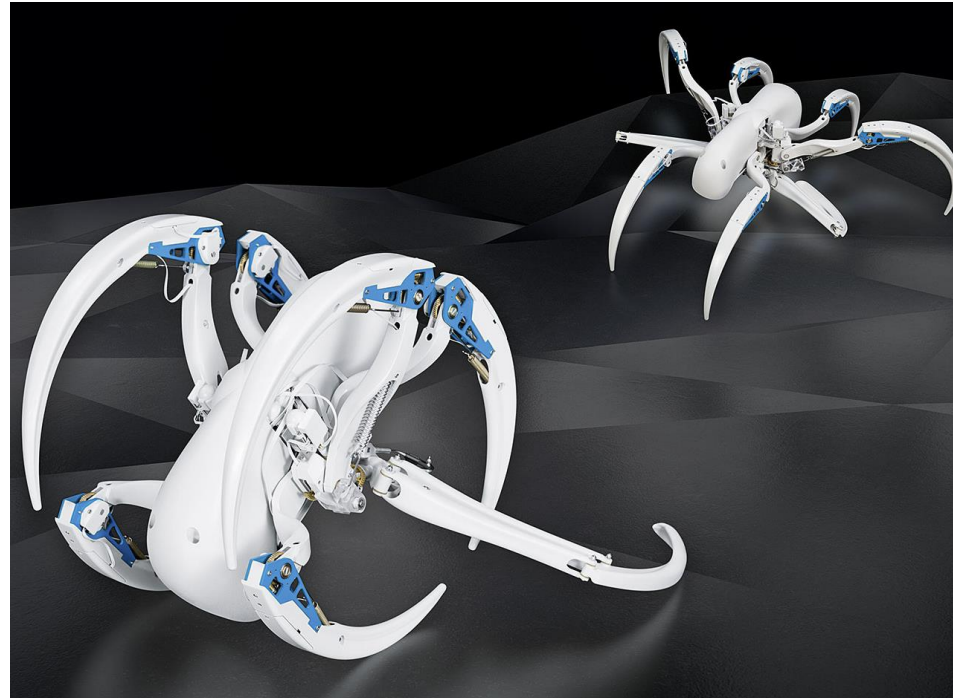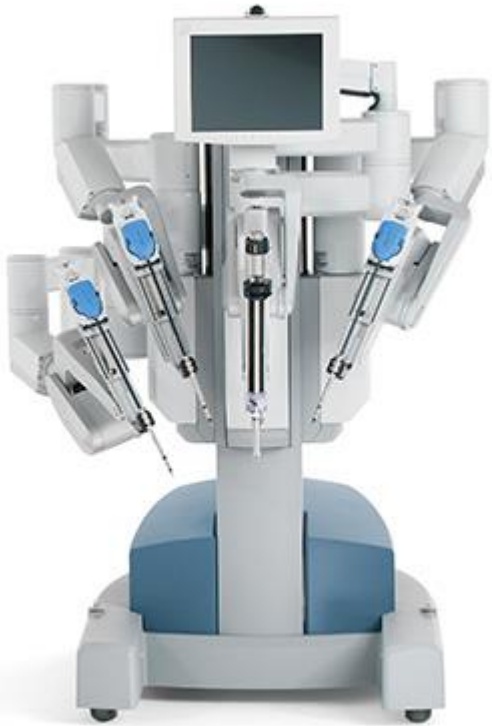


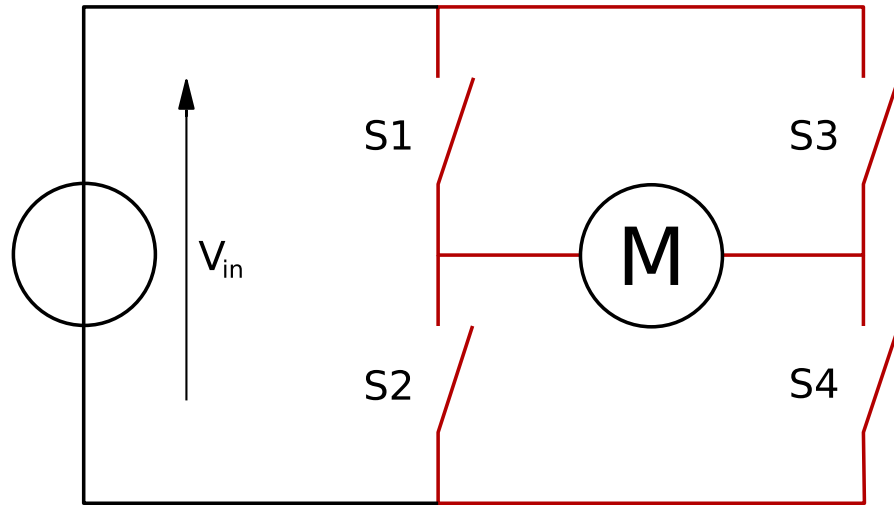

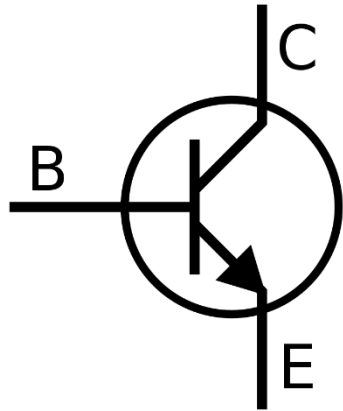- A circuit that allows control over the direction of the applied voltage to the motor
- Traditional switches are mechanical components
- Implementation of a electrical switch
- Control of the direction through digital signals
- Utilization of Transistors as electronic switches




NPN Transistor

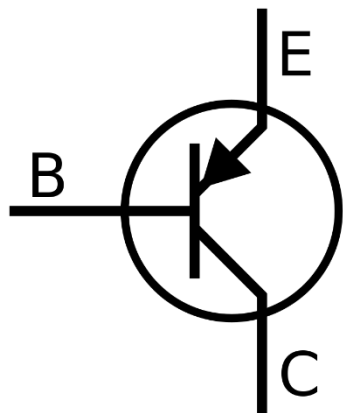


PNP Transistor

- Fundamental semiconductor component in all electronic devices
- Can amplify AC signals (analog circuits) or used as a switch (digital circuits)
- Effectively two n-p junctions in cascade mode

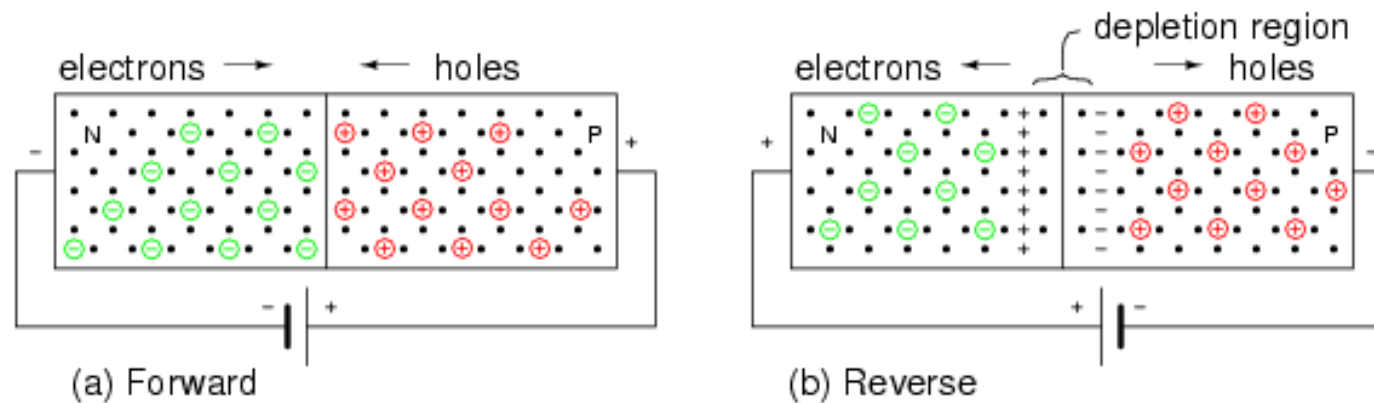- An n-type region with increase free electron concentration
- An p-type region with increase hole (lack of electrons) concentration
- Can effectively conduct or not depending on the applied external voltage (bias)



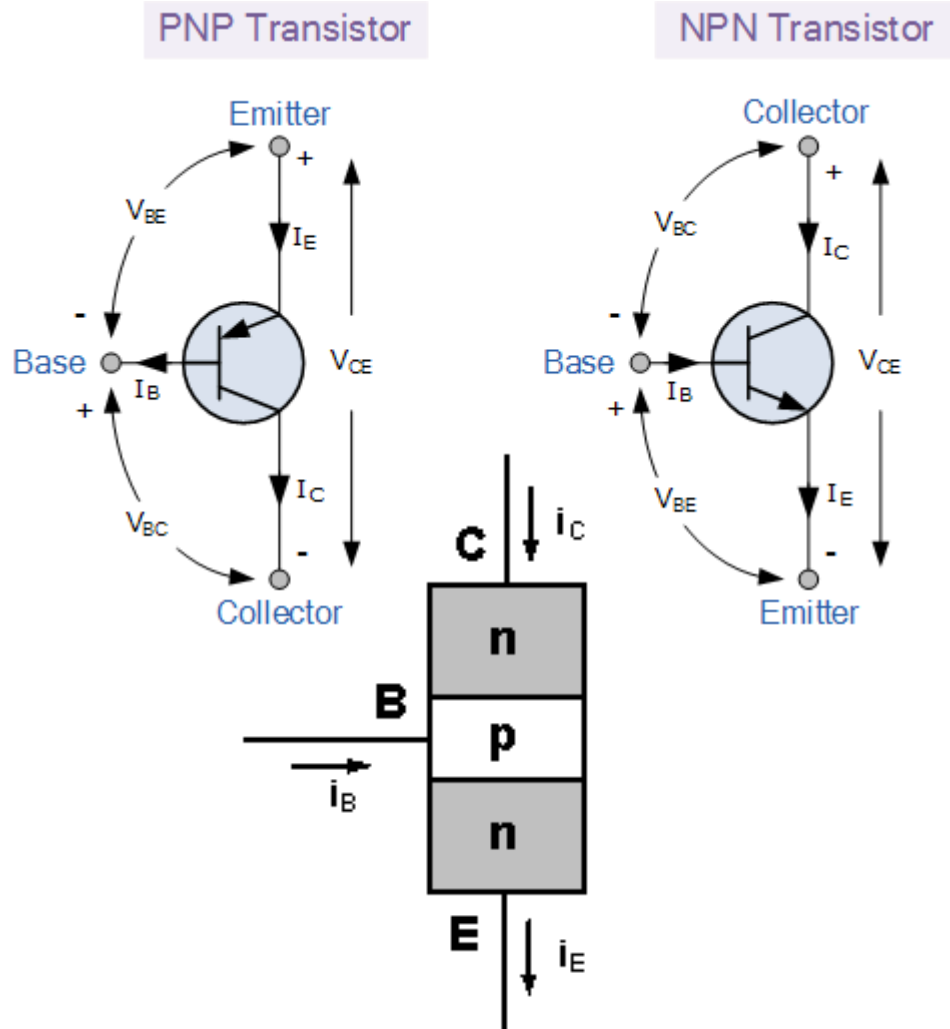

- Four modes of operation: Active, Reverse Active, Cut – Off, Saturation
- **Cut-off:** No current flowing between Collector and Emmitter. **CE contact acts as an open switch.**
- **Saturation:** Currents I_C and I_E are equal. The current flowing between CE contacts is independent of the voltages applied. **CE contact acts as a closed switch.**


NPN Transistor

	Voltage	
Operation Mode	V_{BE}	V_{BC}
Active	positive	negative
Reverse Active	negative	positive
Saturation	positive	positive
Cut-off	negative	negative

PNP Transistor


	Voltage	
Operation Mode	V_{BE}	V_{BC}
Active	negative	positive
Reverse Active	positive	negative
Saturation	negative	negative
Cut-off	positive	positive

H-Bridge circuit

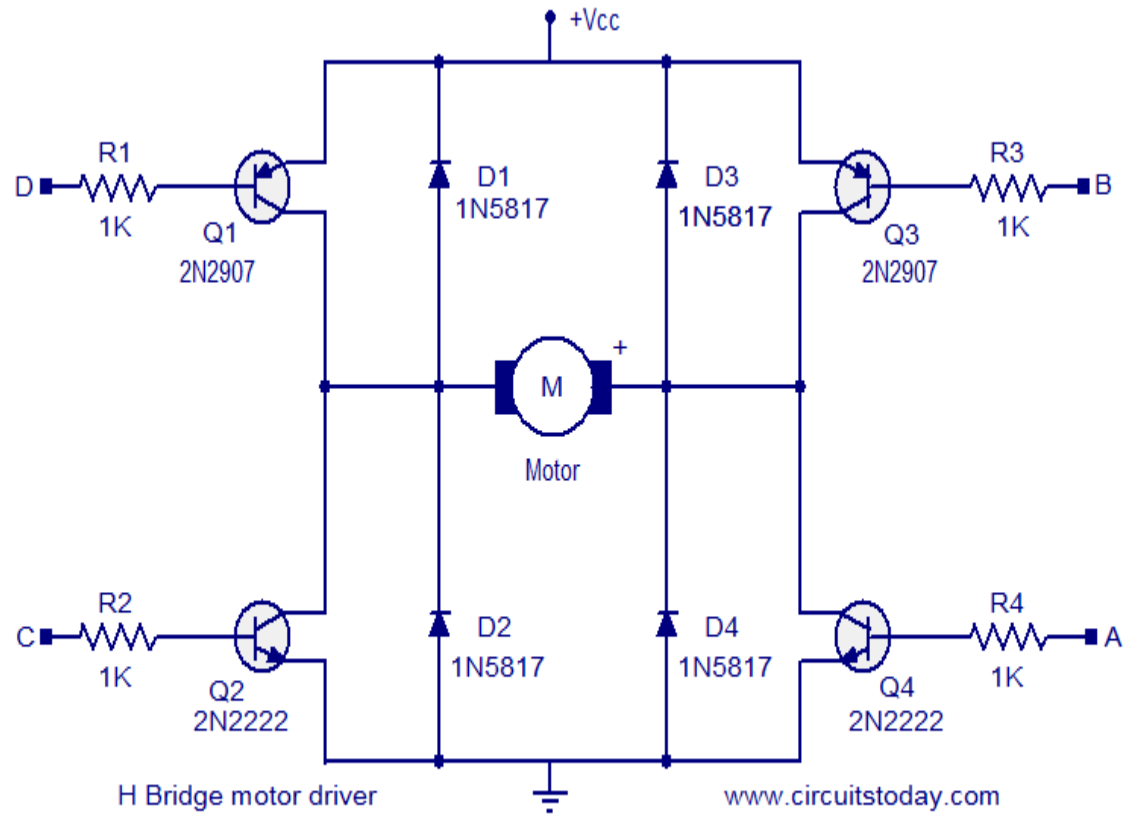

- Simplest implementation of the H-Bridge
- Application of digital signals on inputs A-D to “open” or “close” the transistors
- Resistances $R_1 - R_4$ reduce the input current
- Diodes $D_1 - D_4$ are used as protection to prevent unwanted currents

	Input Voltage V_B	
Transistor Type	Low	High
NPN	Open	Close
PNP	Close	Open

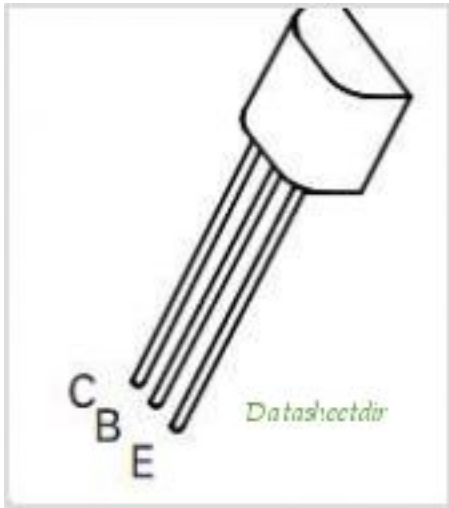

- 5V max PMDC-Motor
- ZTX751 PNP Transistor, 2 A, 60 V
- ZTX651 NPN Transistor, 2 A, 60 V
- 1N4001 Diode, 50V 1A
- Hall Effect Sensor
- 1k Ω resistors